

ELEC 301 MINI PROJECT 4

Yi-Chen Lin - 48861785

1. Objective
2. Introduction
3. Project-Question
4. Reference

List of Figures

Figure 3.1.1 Bode Plot

Figure 3.1.2 Phase Plot

Figure 3.1.3 Oscillation at 10kHz

Figure 3.1.4 Low pass Circuit

Figure 3.1.5 Poles on Plane

Figure 3.1.6 $A_m = 2.5$

Figure 3.1.7 $A_m = 3$

Figure 3.1.8 $A_m = 3.5$

Figure 3.2.1 29k Resistor

Figure 3.2.2 29.03k Resistor

Figure 3.3.1 The Feedback Circuit (In open loop)

Figure 3.3.2 Wave of Varying R_{b2}

Figure 3.3.3 Steady Bode and Phase plot

Figure 3.3.4 100K R_f Bode and Phase Plot

Figure 3.3.5 Varying R_f Bode and Phase Plot

1. Objective

Familiarise and understand the characteristics of several multi-transistor amplifiers/circuits.

2. Introduction

Testing a cascode amplifier, an amplifier consisting of a common-base stage followed by a common-collector stage in cascade, an Op-Amp, and an AM modulator

3. Project-Questions

3.1 Part A

Given information

$$H(s) = A_M \frac{\frac{1}{(RC)^2}}{s^2 + s\left(\frac{3-A_M}{RC}\right) + \frac{1}{(RC)^2}} \quad A_M = 1 + \frac{R_2}{R_1} \quad R = R_1 + R_2 = 10k\Omega$$

With given filter a 3dB frequency of 10kHz, and from the transfer function $\omega = \frac{1}{(RC)} = 2\pi f$

$$C = \frac{1}{R\omega} = \frac{1}{10k\Omega * (2\pi * (10kHz))} = 1.59nF$$

As we know from the 2nd order butterworth filter, the characteristic polynomial appears to be

$$s^2 + \sqrt{2} * s + 1$$

Thus, we can find the A_M

$$A_M = 3 - \sqrt{2} = 1.586$$

By solving equation of

$$R_1 + R_2 = 10k\Omega \text{ and } A_M = 1 + \frac{R_2}{R_1}$$

We got

$$R_1 = 6306\Omega \text{ and } R_2 = 3693\Omega$$

Which is $R_1 = 6.2k\Omega$ and $R_2 = 3.9k\Omega$ in standard value


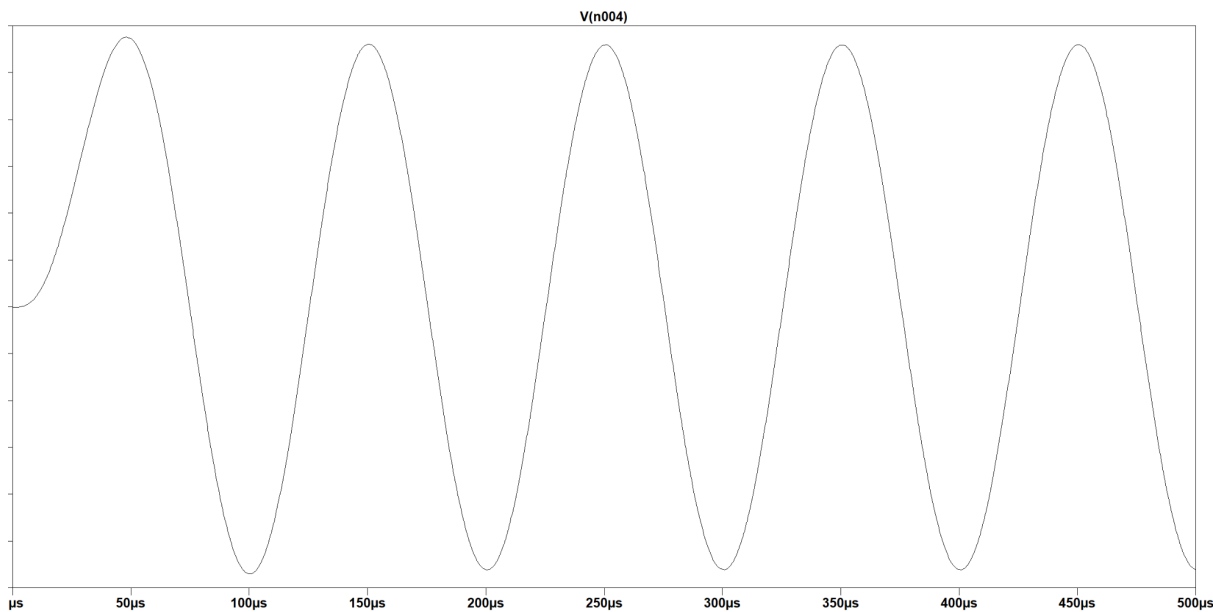
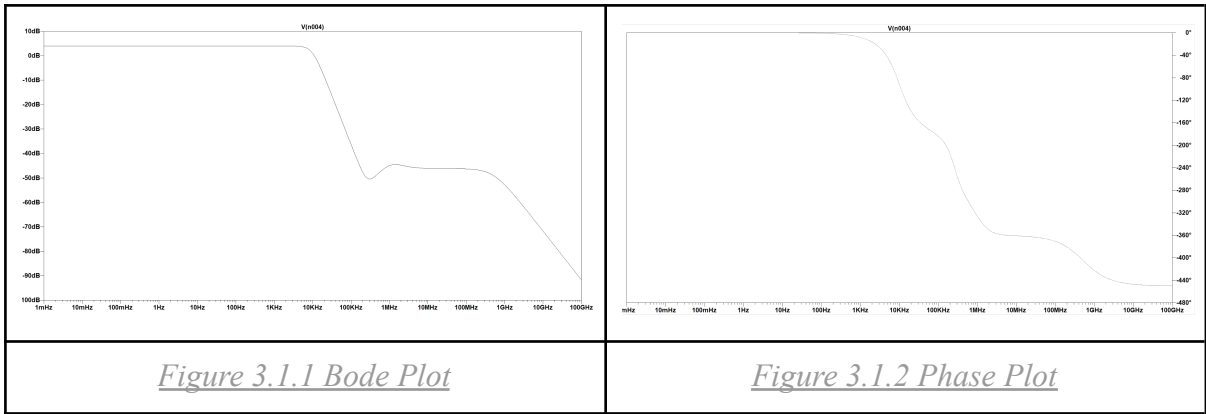


Figure 3.1.3 Oscillation at 10kHz

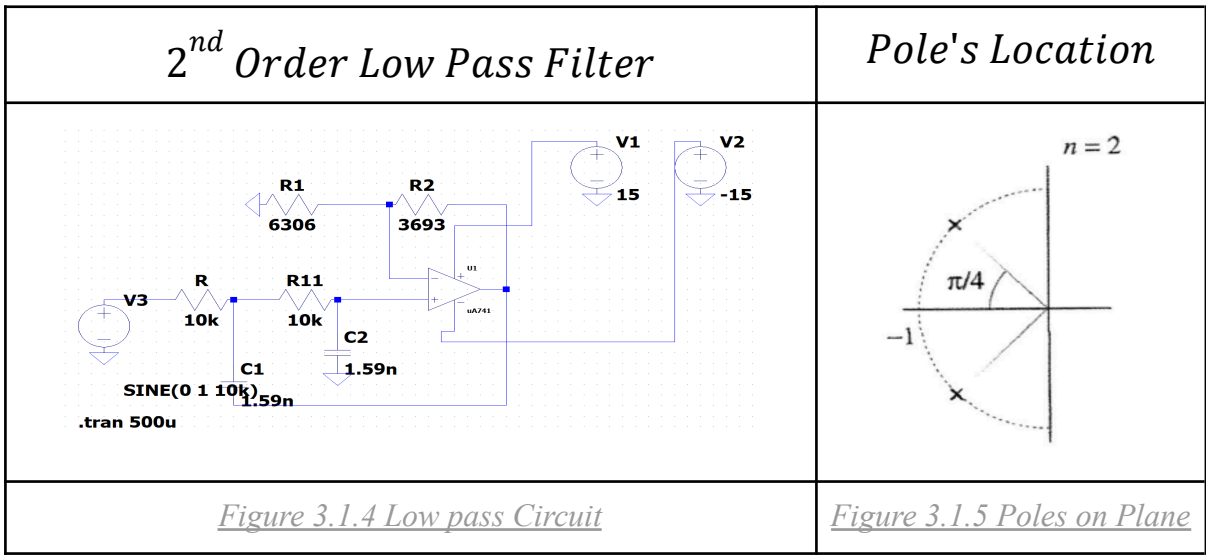At what value of AMdoes your circuit start t



Root Locus Plot

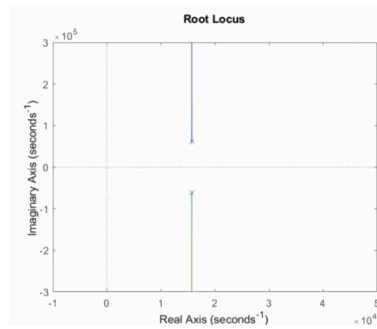


Figure 3.1.6 $A_m < 3$ (2.5)

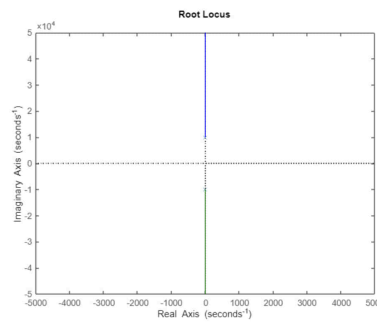


Figure 3.1.7 $A_m = 3$


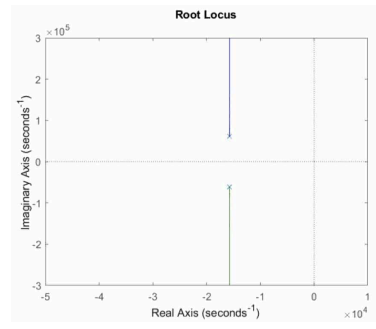


Figure 3.1.8 $A_m > 3$ (3.5)

3.2 Part A

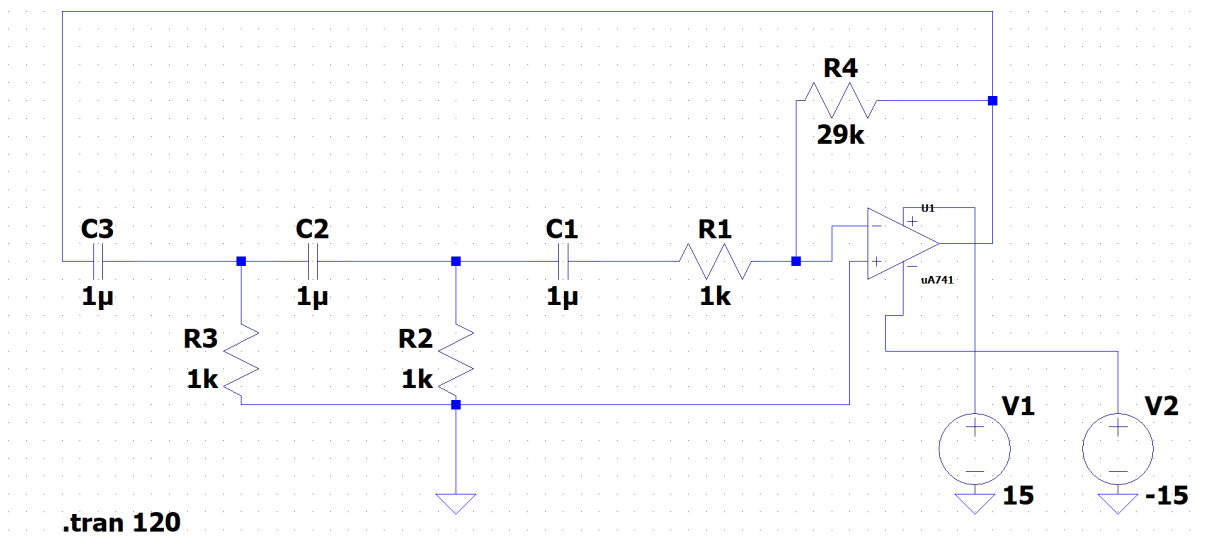

By running the simulation, we found that the breakdown occurs when the value of $29k$ resistor becomes $29.02k$. Rather than the flat continuous voltage, it leads to a sudden breakdown

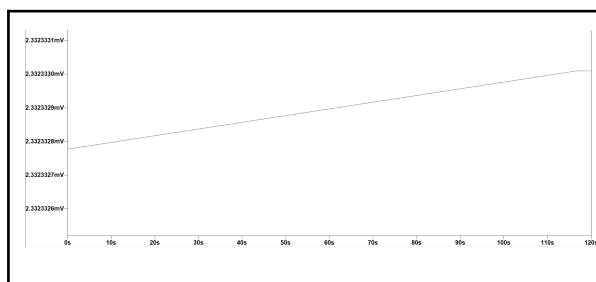


Figure 3.2.1 $29k$ Resistor

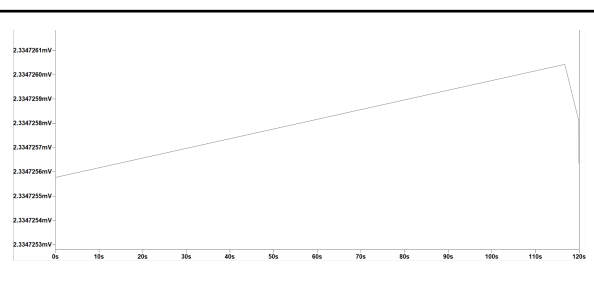


Figure 3.2.2 $29.02k$ Resistor

Use $f = \frac{1}{2\pi RC \sqrt{6}}$ for the frequency calculation and measuring the bode plot out while changing resistors and capacitors values gives us the following results.

| | | | |
|-----------------|------------|--------------|------------|
| C | $1\mu F$ | $0.5\mu F$ | $2\mu F$ |
| R | $1k\Omega$ | $0.5k\Omega$ | $2k\Omega$ |
| $f_{Calculate}$ | 65 Hz | 260 Hz | 16.2 Hz |
| $f_{Measured}$ | 65 Hz | 259 Hz | 16 Hz |
| Error | 0 % | 0.38 % | 1.23% |

At the operating frequency, the three RC filters introduce an attenuation factor of $\frac{1}{29}$. To achieve unity gain, the inverting amplifier's gain is set to 29, satisfying the Barkhausen criterion for sustained oscillations. When the circuit has unity gain, it results in a pair of complex conjugate poles lying on the imaginary axis, which explains the sustained oscillation. In some cases, it may be necessary to slightly increase the resistance (denoted as 29R) to compensate for OpAmp non-idealities. These non-idealities can shift the poles closer to the left half-plane, and adjusting the resistance helps move the poles closer to the imaginary axis to maintain stable oscillation.

3.3 Part A

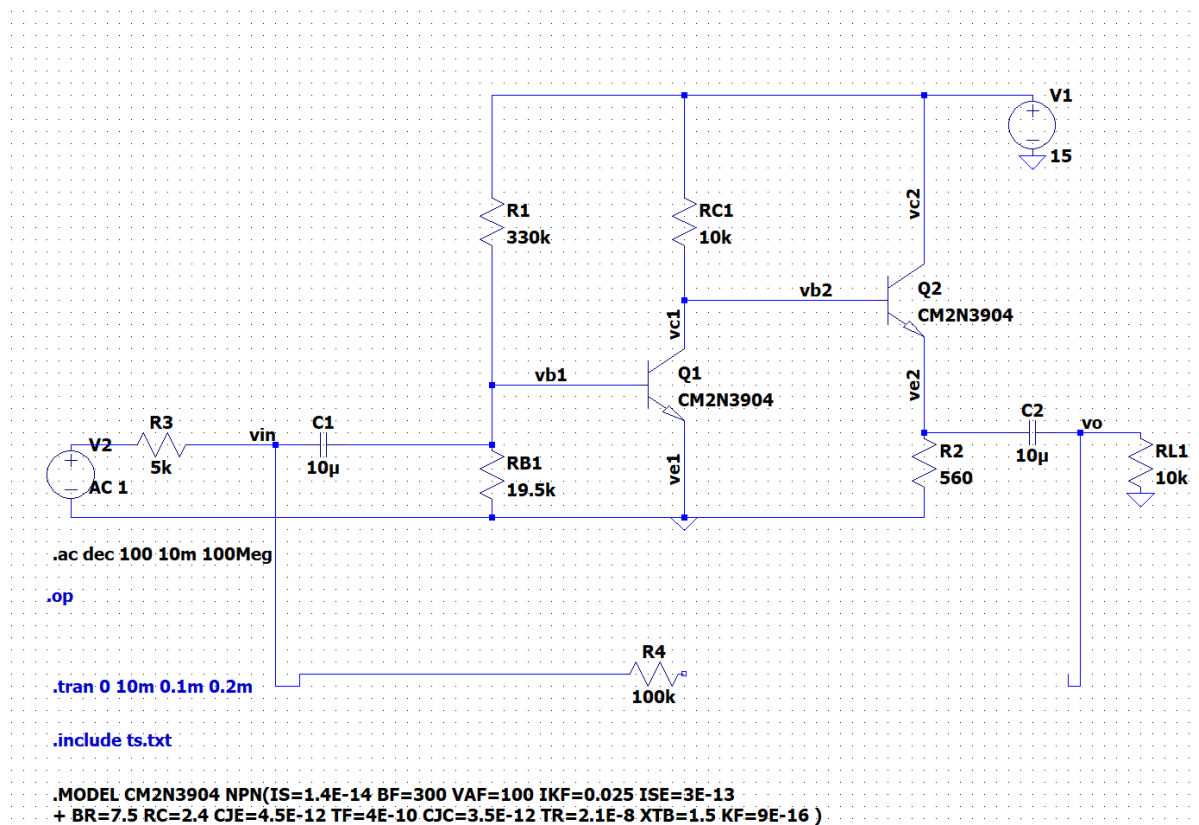


Figure 3.3.1 The Feedback Circuit (In open loop)

To begin with, we use the .step param on RB1 located on the image above to sweep and find the greatest open loop gain by opening the feedback circuit at the same time.

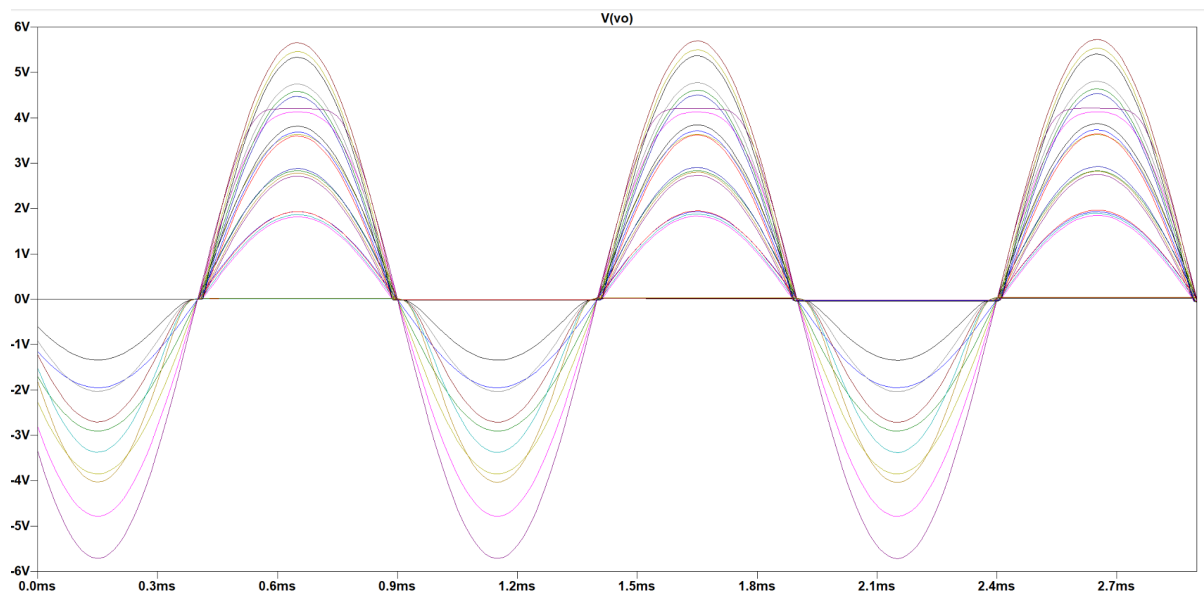


Figure 3.3.2 Wave of Varying Rb2

From the above plot, we found that the final value ends up around 19.5 k Ω

3.3.1 DC biasing points

| | V_C | V_B | V_E | I_C | I_B | I_E | h_{fe} | g_m | r_π |
|----|-------|-------|-------|--------|--------|-------|----------|-------|---------|
| Q1 | 1.9V | 0.65V | 0V | 1.32mA | 10.9uA | 1.3mA | 120 | 0.053 | 2.3k |
| Q2 | 15V | 1.9V | 1.1V | 2.1mA | 14.5uA | 1.8mA | 141 | 0.088 | 1.6k |

3.3.2 Open Loop Response

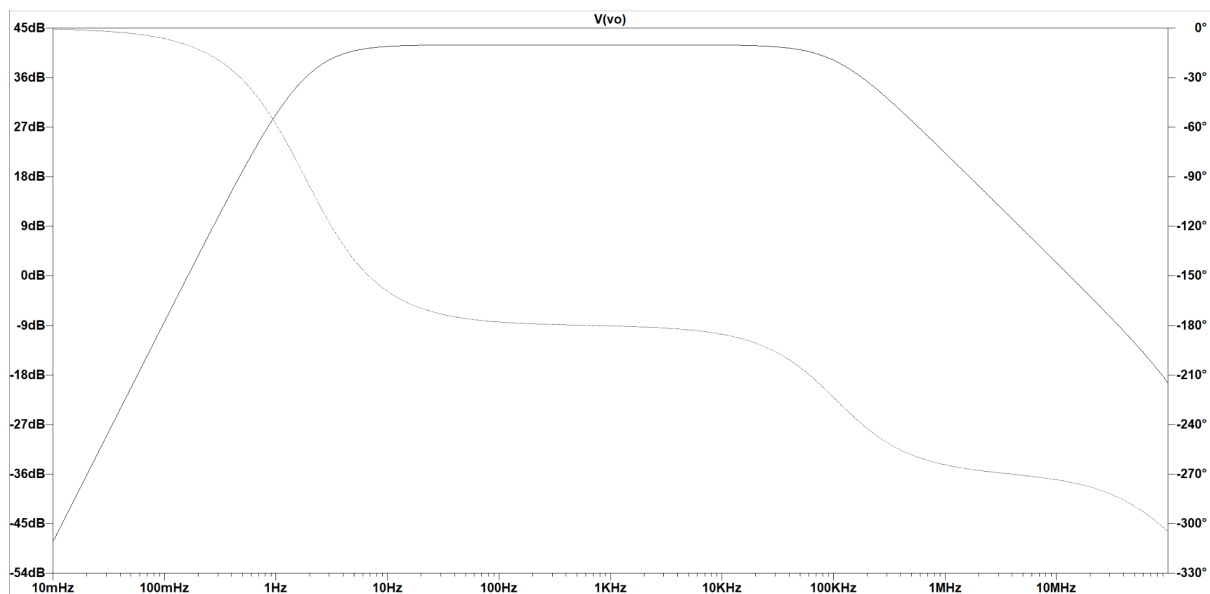


Figure 3.3.3 Steady Bode and Phase plot

| ω_{L3dB} | ω_{H3dB} | A_M | R_{in} measured | R_{out} measured |
|-----------------|-----------------|-------|-------------------|--------------------|
| 2.89Hz | 88.4kHz | 42.22 | 2.42k Ω | 65.2 Ω |

With the closed loop condition, we use shunt-shunt topology with Y parameter to solve for the variables and gain using $R_f = 100k\Omega$

| | |
|--|--|
| | $\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$ |
|--|--|

$$y_{11} = \frac{I_1}{V_1} \big|_{V_2=0} \quad y_{12} = \frac{I_1}{V_2} \big|_{V_1=0} \quad y_{22} = \frac{I_2}{V_2} \big|_{V_1=0}$$

$$y_{11} = \frac{1}{R_f} \quad y_{12} = \frac{-1}{R_f} \quad y_{22} = \frac{1}{R_f}$$

We neglect $y_{21} = \frac{I_2}{V_1} \big|_{V_2=0}$ since it is usually small and find feedback gain using the open loop gain $A = R_s A_m$ and $\beta = y_{12} = 10 \mu S$

$$A_f = \frac{A}{1 + \beta A}$$

And the adjusted value with feedback is listed simply as

$$A = \frac{V_o}{I_s} = \frac{V_o}{V_s/R_s} = \frac{10^{\frac{42.05}{20}}}{1/5000} = -633k \frac{V}{A}$$

$$A_f = \frac{633k}{1 - 10^{-5} * -633k} = -86.36k \frac{V}{A}$$

Frequency at 3dB point


$$f_{L3dB} = \frac{2.89}{1 + 10^{-5} * 633k} = 0.394 \text{ Hz}$$

$$f_{H3dB} = (1 + 10^{-5} * 633k) * 88.4k = 648 \text{ kHz}$$

Resistors after the feedback implemented

$$R_{inNEW} = \frac{2.42k}{1 - 10^{-5} * -633k} = 330 \Omega$$
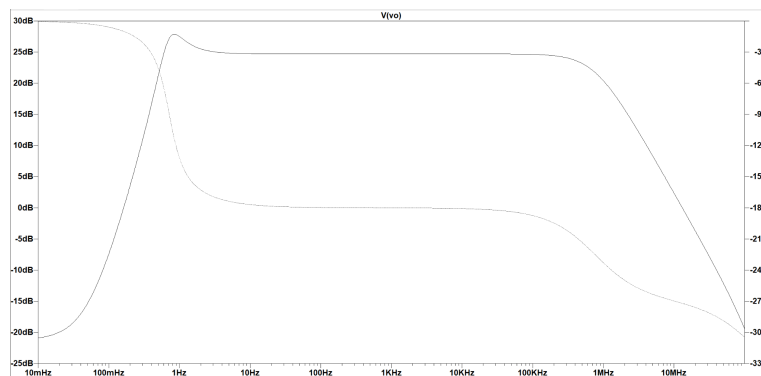
$$R_{outNEW} = \frac{65.2}{1 - 10^{-5} * -633k} = 8.89 \Omega$$



unclear axis -2

Figure 3.3.4 100K Rf Bode and Phase Plot

3.3.3

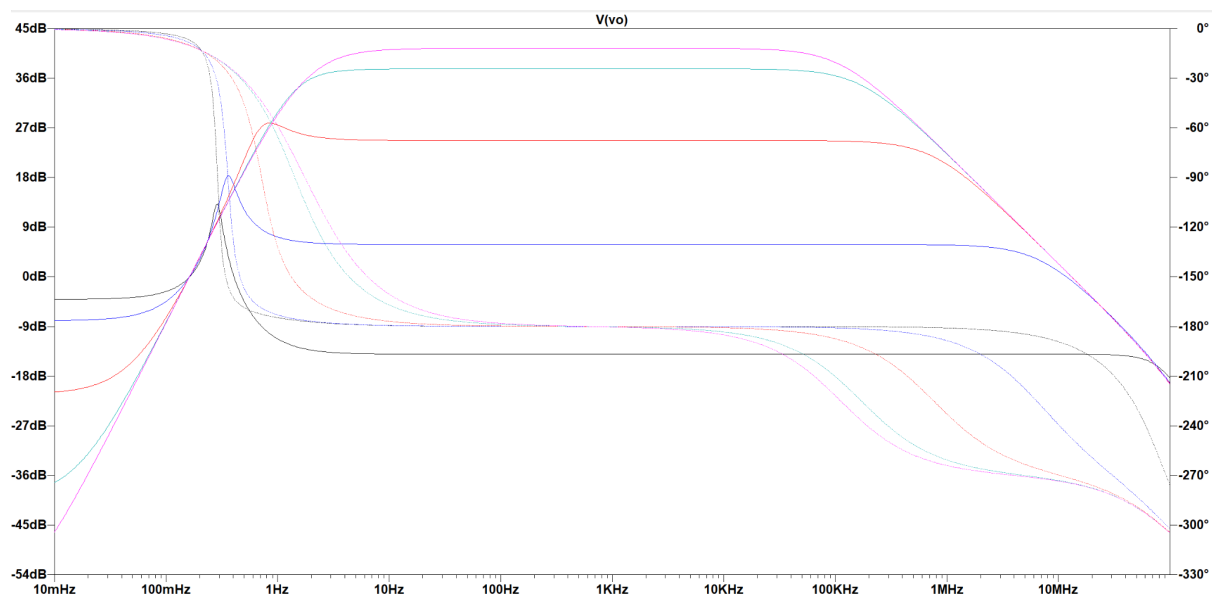


Figure 3.3.5 Varying Rf Bode and Phase Plot

Rewrite the feedback formula

$$A_f = \frac{A}{1+A\beta} \Rightarrow \beta = \frac{1}{A_f} - \frac{1}{A} = \frac{1}{A_{vf} * R_s} - \frac{1}{A}$$

| R_f | Measured A_{vf} | Calculated β | Measured β |
|---------------|-------------------|--------------------|----------------------------|
| 1k Ω | -14.05 | -10^{-3}S | $-1.005 * 10^{-3}\text{S}$ |
| 10k Ω | 5.86 | -10^{-4}S | $-1.003 * 10^{-4}\text{S}$ |
| 100k Ω | 24.75 | -10^{-5}S | $-1.002 * 10^{-5}\text{S}$ |
| 1M Ω | 37.85 | -10^{-6}S | $-1.002 * 10^{-6}\text{S}$ |
| 10M Ω | 41.61 | -10^{-7}S | $-1.01 * 10^{-7}\text{S}$ |

3.3.4

Determine the R_{in} and R_{out} with 1kHz and running R_f in list and predict the feedback with

$$R_{if} = \frac{R_i}{1+A\beta} \Rightarrow 1 + A\beta = \frac{R_i}{R_{if}}$$

$$R_{of} = \frac{R_o}{1+A\beta} \Rightarrow 1 + A\beta = \frac{R_o}{R_{of}}$$

| R_f | Measured R_{if} | Measured R_{of} | Feedback R_{if} | Feedback R_{of} | Predicted $1+A\beta$ |
|---------------|-------------------|-------------------|-------------------|-------------------|----------------------|
| 10k Ω | 26.2 Ω | 1.14 Ω | 96.6 | 55.7 | 65 |
| 100k Ω | 240.2 Ω | 8.71 Ω | 10.6 | 7.29 | 7.4 |
| 1M Ω | 1304 Ω | 38.4 Ω | 1.98 | 1.64 | 1.6 |

Following our simulation, we found out that As the value of R_f increases, the output feedback will be close to our predicted feedback following the above equation. And as the table displayed, the R_{of} is the one we use to estimate feedback instead of the R_{if}

3.3.5

By setting $R_f = \infty$ we will lead to $\beta = 0$, which has no feedback in the circuit leading the amplifier turns into an open loop with $1+A\beta=1$

| R_c | A_v | β | $1 + A\beta$ |
|----------------|-----------------------|---------------------------------------|--------------|
| 9.9k Ω | -126.1 $\frac{V}{V}$ | -2.4 * 10 ⁻⁹ $\frac{A}{V}$ | 1.003 |
| 10k Ω | -126.62 $\frac{V}{V}$ | -34 * 10 ⁻¹¹ $\frac{A}{V}$ | 1 |
| 10.1k Ω | -127.2 $\frac{V}{V}$ | 3 * 10 ⁻⁹ $\frac{A}{V}$ | 0.998 |

and with 100k Ω , we used the predicted feedback from previous part $1+A\beta = 7.39$

| R_c | A_{vf} | β | $1 + A\beta$ |
|----------------|----------------------|--|--------------|
| 9.9k Ω | -17.22 $\frac{V}{V}$ | -11.0 * 10 ⁻⁶ $\frac{A}{V}$ | 7.41 |
| 10k Ω | -17.26 $\frac{V}{V}$ | -10.02 * 10 ⁻¹¹ $\frac{A}{V}$ | 7.40 |
| 10.1k Ω | -17.28 $\frac{V}{V}$ | -9.01 * 10 ⁻⁹ $\frac{A}{V}$ | 7.39 |

In your report compare this value with your expected value using the measured values of A and β

As seen from the above calculation and experiments with the smaller values of R_f , the intermediate frequency shows higher gain compared to the lower frequencies. This behavior can be attributed to the frequency dependence of the amplifier and the feedback network. At lower frequencies, the capacitive reactance is higher, which causes the circuit to produce a larger overall gain.

4. References

1. ELEC 301 Course Notes
2. A. Sedra and K. Smith, "Microelectronic Circuits", 8th (or higher) Ed., Oxford University Press, New York.
3. LTSPICE User's Tutorial
4. Canvas Transistor Documents
5. [2N3904 datasheet](#)